

KATHMANDU UNIVERSITY
Department of Electrical and Electronics Engineering
ELEMENTS OF ENGINEERING II - ENGG112
SECOND INTERNAL

Full Marks: 20
Time: 50 minutes

[ATTEMPT ANY 4 QUESTIONS]

Question 1. For the network of Figure. 1, find the current I , the voltage V_C , and the average power delivered to the network. [5]

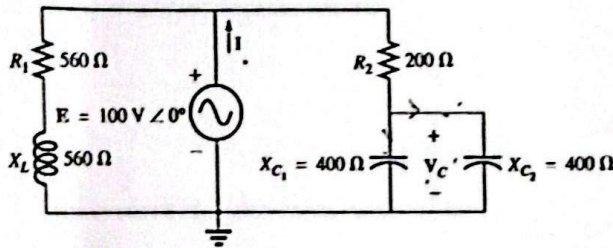


Figure 1

Question 2. Find the average value and RMS of AC signal in Figure 2. [2+3]

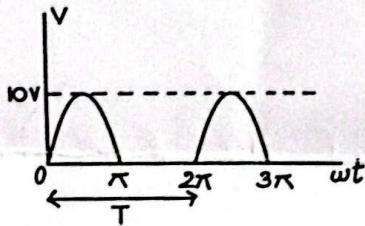


Figure 2

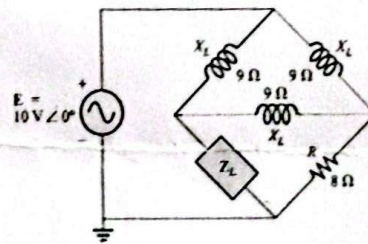


Figure 3

Question 3. In network shown by figure 3, find the load impedance in the network for maximum power to the load and find the maximum power delivered. [5]

Question 4. Derive the expression of resonating frequency in series RLC circuit. Write an equation for Bandwidth, Quality factor and half power frequencies. [2+1+1+1]

Question 5. A star connected 3-phase load has a resistance of 6 ohm and inductive reactance of 8 ohm in each branch. A line-to-line voltage of 220V is supplied to the 3-phase load through a 3-phase source. Find the voltage across each branch, line currents and total active power. (Write the voltage across each branch and line currents in phasor form). [2+2+1]

$V_{\phi} = 0$
 $J_{\phi} = ?$
 $V_{\phi} = \sqrt{3} V_{\phi}$
 $I_L = 3\phi$
 $P = \sqrt{3} 3\phi V_{\phi} \cos \theta$